

PHY 202 TEST 1 – ELECTRIC CIRCUITS & ELECTRONICS
Answer all questions


Remove Watermark

Wondershare
PDFelement


30 Minutes

1. (a) Define electric current. [1 mark]
(b) Differentiate between a.c. and d.c. [1 mark]
(c) The circuit (Fig. 1) shows a battery of e.m.f. 6.0 V connected to a switch and to two resistors in parallel, each of resistance $3.0\ \Omega$. The switch S is closed for a period of 5.0 minutes. Calculate:

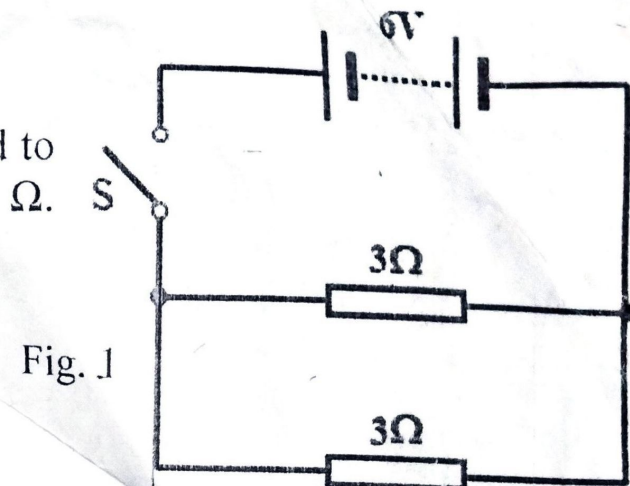- (i) the current through each resistor. [2 marks]
(ii) the current through the battery. [2 marks]
(iii) the total charge which passes through the battery. [2 marks]
(iv) the energy supplied by the battery. [2 marks]
[© CIE GCE Physics]



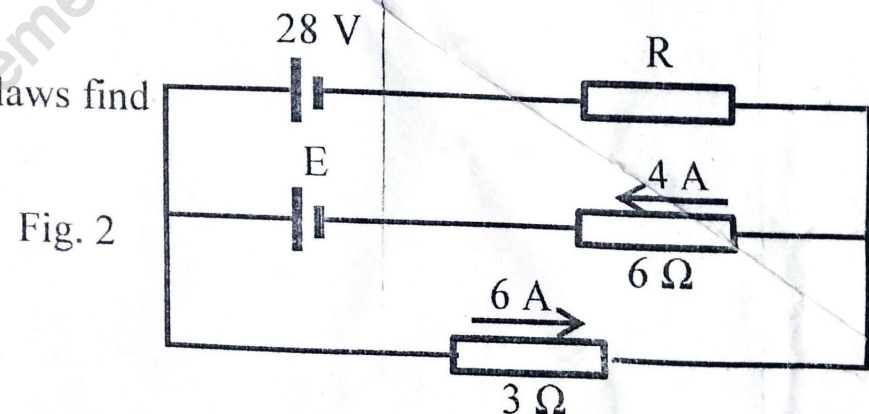2. In the circuit shown in Fig. 2, using Kirchhoff's laws find
(a) the current in resistor R; [3 marks]
(b) the resistance R; [4 marks]
(c) the unknown e.m.f. E. [3 marks]




3. (a) State one difference between electrical resistance and reactance. [1 mark]
(b) An alternating source of 10.0 V and frequency 100 Hz is connected in series with a $5\ \Omega$ resistor and 20 mH inductor.
(i) Draw the circuit diagram of the arrangement. [1 mark] Calculate the:
(ii) reactance of the inductor. (iii) impedance of the circuit. (iv) potential difference across the inductor. [8 marks]

PHY 202 TEST 1 MARK SCHEME 2021-2022

1(a) Electric current is the rate of flow of electric charges ①

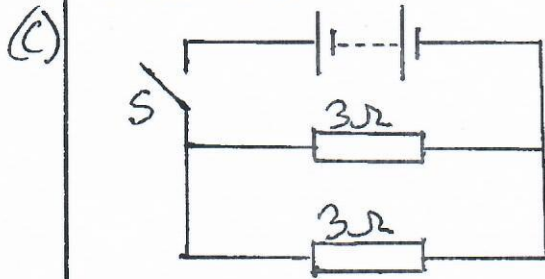(b) a.c. is characterised by periodical change in direction of current while d.c. is characterised by unidirectional flow of current. ①



(i) p.d. across each resistor is 6V


$$I = \frac{V}{R} = \frac{6V}{3\Omega} = 2A \text{ each } ②$$

(ii) current I through the battery

$$I = 2A + 2A = 4A \text{ } ②$$

$$(iii) Q = It = 4 \times 5 \times 60 = 1,200C \text{ } ②$$
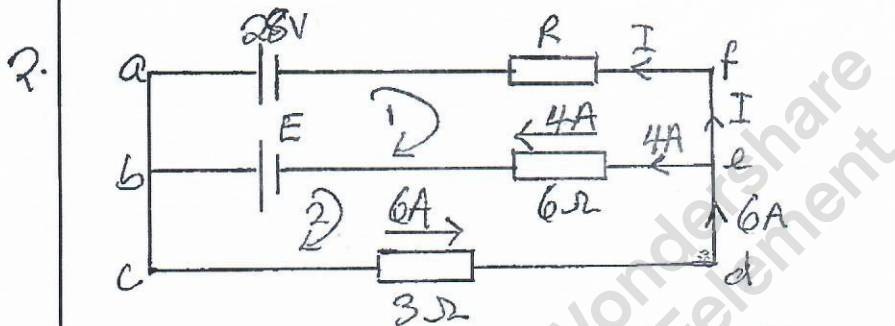
$$(iv) E = IVt = 4 \times 6 \times 5 \times 60 = 7,200J \text{ } ②$$



(a) At junction e: $I + 4 = 6$ ①

$$I = 6 - 4 = 2A \text{ } ①$$

$$I = 2A \text{ } ①$$

(b) using loop 2: bledcb ①

$$-E + 4(6) + 6(3) = 0 \text{ } ①$$

$$-E + 24 + 18 = 0 \text{ } ①$$

$$24 + 18 = E$$

$$E = 42V \text{ } ①$$

(c) using loop 1: afedba ①

$$-28 + 2(R) - 4(6) + E = 0 \text{ } ①$$

$$-28 - 24 + 42 + 2R = 0$$

$$-10 + 2R = 0$$

$$2R = 10$$


$$R = 10/2$$

$$R = 5\Omega \text{ } ①$$

30) — Resistance dissipates electrical energy, reactance does not.

Any 1 x 1 mk = 1 — Reactance value depends on frequency of a.c; resistance does not.

(b) (i)

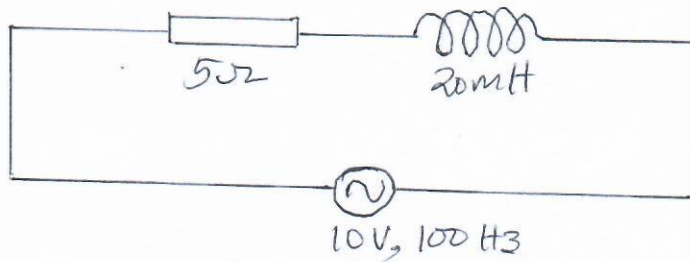

Complete diagram
with the right
circuit symbols
①

(ii) $X_L = \omega L = 2\pi fL = 2\pi \times 100 \times 20 \times 10^{-3} = \underline{12.6 \Omega}$ ①

(iii) $Z = \{R^2 + X_L^2\}^{1/2}$ ①
 $= \{5^2 + 12.6^2\}^{1/2}$
 $= \{25 + 158.76\}^{1/2}$

$Z = \{183.76\}^{1/2}$
 $Z = \underline{13.6 \Omega}$ ①

(iv) $I = V/Z = \frac{10V}{13.6 \Omega} = \underline{0.735A}$ ①

$V_L = IX_L = 0.735 \times 12.6 = \underline{9.3V}$ ①